

R09

Code No: 09A40204

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY, HYDERABAD

B.Tech II Year II Semester Examinations, June-2014

SWITCHING THEORY AND LOGIC DESIGN

(Common to BME, EEE, ECE, ETM)

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

1.a) Convert the following numbers into the corresponding bases.

- i) $(53)_{10} = (\quad)_2$
- ii) $(231)_8 = (\quad)_{10}$
- iii) $(1101101)_2 = (\quad)_8$
- iv) $(4D.56)_{16} = (\quad)_2$

b) Encode the following message bits into 7-bit even parity hamming code.

- i) $(1011)_2$
- ii) $(1100)_2$

2.a) Simplify the following Boolean expressions to minimum number of literals using Boolean algebra.

- i) $A'C' + ABC + AC' + AB'$
- ii) $A'B(D' + CD) + B(A + A'CD)$

b) Find the complement of the following functions.

- i) $(A'B + CD)E' + E$
- ii) $XY' + X'Y$

3. Simplify the following function using Tabular method

$$F(A,B,C,D) = \Sigma(0,1,2,3,4,6,9,10) + d(7,11,12,13,15).$$

4.a) Implement the following functions using a decoder.

$$F1 = \Sigma(1,3,5,7)$$

$$F2 = \prod(0,2,5,7)$$

$$F3 = \Sigma(3,4,6,7)$$

b) Design a BCD to Excess-3 code converter.

5. Implement the following Boolean functions using PLA

$$F1(A,B,C) = \Sigma m(1,2,4,6)$$

$$F2(A,B,C) = \Sigma m(0,1,6,7)$$

$$F3(A,B,C) = \Sigma m(2,6)$$

$$F4(A,B,C) = \Sigma m(1,2,3,5,7).$$

6.a) Draw the characteristic table of JK flip flop and obtain its characteristic equation.

b) Realize JK Flip flop using SR Flip flop.

- 7.a) Discuss the capabilities and limitations of Finite State Machine.
b) Minimise the following machine using partition method by writing necessary steps involved.

PS	NS,Z	
	x = 0	x = 1
A	E,0	D,1
B	F,0	D,0
C	E,0	B,1
D	F,0	B,0
E	C,0	F,1
F	B,0	C,0

- 8.a) What are the basic elements of ASM chart?
b) Design a binary multiplier and its control logic by drawing ASM chart and realize the same using decoder, MUX and D Flip-Flops.

