

Note: This question paper contains two parts A and B.
Part A is compulsory which carries 25 marks. Answer all questions in Part A.
Part B consists of 5 Units. Answer any one full question from each unit.
Each question carries 10 marks and may have a, b, c as sub questions.

PART - A**(25 Marks)**

- 1.a) State KVL and underlying logic. [2]
- b) Distinguish between dependent and independent sources. [3]
- c) What is meant by locus diagram? [2]
- d) Find the power delivered from a sinusoidal source to a resistor R . [3]
- e) Write the expression for equivalent inductance of series connected magnetically coupled coils. [2]
- f) What is the significance of power factor? [3]
- g) Give the properties of tree in a graph. [2]
- h) Write some applications of maximum power transfer theorem. [3]
- i) Define super node. Indicate the super node in a network. [2]
- j) State Millman's theorems for D.C excitation. [3]

PART - B**(50 Marks)**

- 2.a) Distinguish between star (3 and 4-wire) and delta connections.
- b) What values must R_1 and R_2 have when $I_1 = 4A$ and $I_2 = 6 A$ both charging in the circuit of Figure 1.

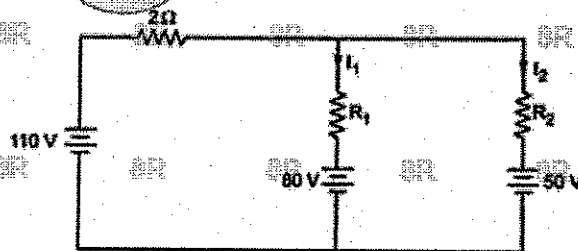


Figure 1

- c) An electric heater consumes 1.8MJ when connected to a 250V supply for 30 minutes. Find the power rating of the heater and the current taken from the supply. [2+4+4]

OR

- 3.a) If a unit step voltage is given to an inductor of 1H , then what is the current flowing through it?
- b) Find the current flowing in the $3\ \Omega$ resistor for the network shown in Figure 2. Find also the potential difference across the $10\ \Omega$ and $20\ \Omega$ resistors.

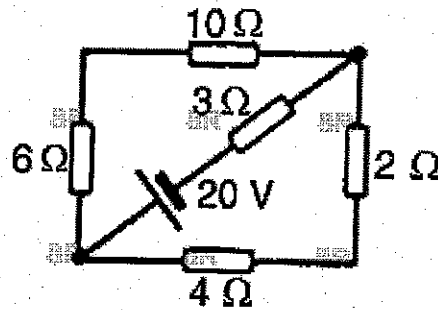


Figure 2

- c) What are active and passive elements? Give examples of each. [2+5+3]
- 4.a) Find the ac power entering an inductor L .
- b) A two-element series circuit has average power 940W and power factor 0.707 leading. Determine the circuit elements if the applied voltage is $v = 99.0 \cos(6000t + 30^\circ)\text{V}$.
- c) Write the expression for the impedance of the RC circuit in rectangular and polar form. [2+4+4]
- OR
- 5.a) Find the total instantaneous power $p(t)$, the average power P , and the reactive power Q , delivered from $v = (V\sqrt{2})\cos\omega t$ to a parallel RLC combination.
- b) Find the two elements of a series circuit having current $i = 4.24 \cos(5000t + 45^\circ)\text{A}$, power 180W , and power factor 0.80 lagging.
- c) Write the expression for the impedance of the RL circuit in rectangular and polar form. [4+4+2]
- 6.a) Write the characteristics of series resonance.
- b) An average e.m.f of 60V is induced in a coil of inductance 160mH when a current of 7.5A is reversed. Calculate the time taken for the current to reverse.
- c) For a series RL circuit obtain the locus of current as inductance is changed from 0 to ∞ when the applied voltage is constant. [3+4+3]

OR

- 7.a) For the circuit in Figure 3, find the value of ω so that current and source emf are in phase. Also find the current at this frequency.

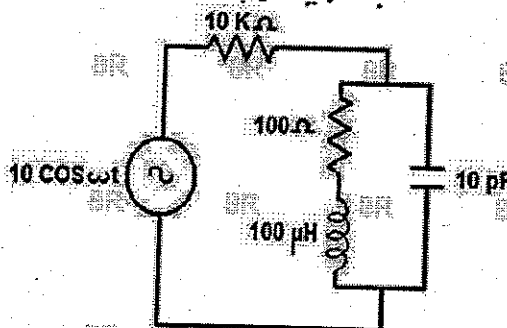


Figure 3

- b) Derive the formula for mutual inductance in terms of coefficient of coupling and self-inductance.
- c) State dot rule for coupled circuit. [4+3+3]

- 8.a) What is a dual network? Give examples.
 b) For the topological graph shown in Figure 4, obtain the fundamental tie-set matrix choosing the tree containing two elements 5 and 6.

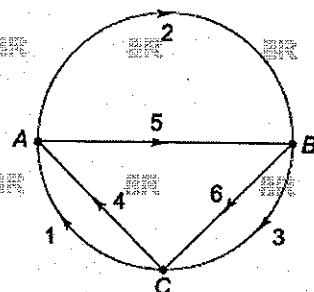


Figure 4

- c) Define and explain the Oriented Graph with an example.

[4+3+3]

OR

- 9.a) For the network shown in Figure 5, draw the graph and tree.

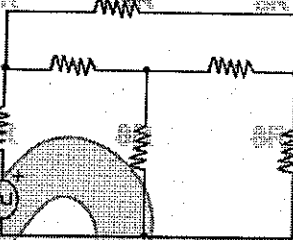


Figure 5

- b) Describe the procedure to construct the dual of a network with an example.
 c) Explain the sub-graph with respect to graph theory.

[3+4+3]

- 10.a) State the steps to solve the Norton's theorem.

- b) Find the value of R_L so that maximum power is delivered to the load resistance shown in Figure 6.

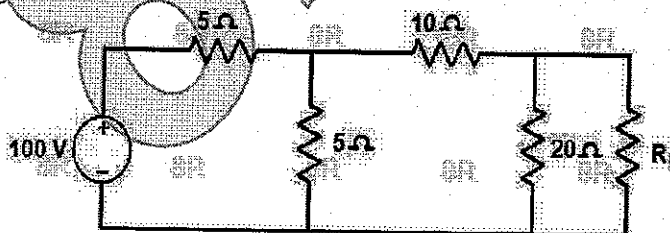


Figure 6

- c) State Tellegen's theorem.

[3+3+4]

OR

- 11.a) State reciprocity theorem.

- b) Find the value of the adjustable resistance R which results in maximum power transfer across the terminals ab of the circuit shown in Figure 7.

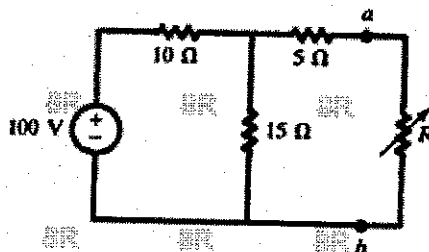


Figure 7

- c) What is the limitation of superposition theorem?

[3+3+4]

